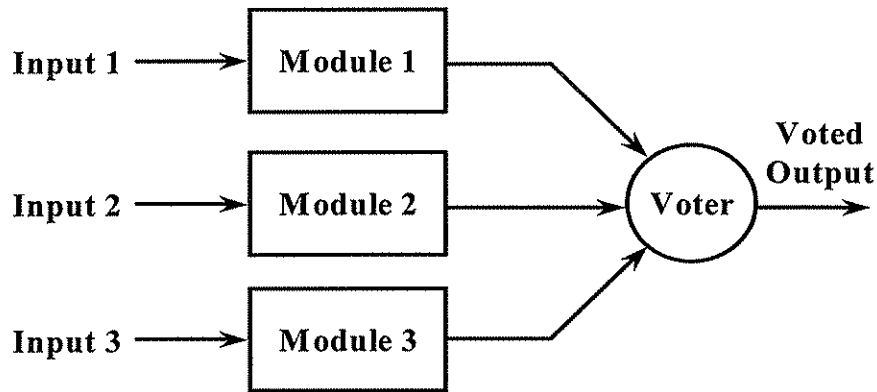


Reliability of TMR



- Reliability of each module: p
- Reliability of the voter: w
- Reliability of TMR?

$$\begin{aligned} R_{\text{TMR}} &= \left[C_3^3 p^3 (1-p)^0 + C_3^2 p^2 (1-p) \right] \cdot w \\ &= \left[p^3 + 3 p^2 (1-p) \right] w \\ &= (3 p^2 - 2 p^3) \cdot w \end{aligned}$$

Where $C_n^k = \binom{n}{k} = \frac{n!}{k!(n-k)!}$ is binomial coefficient.

Reliability of NMR

- Reliability of each module: p
- Reliability of the voter: w
- $N = 2n + 1$
- Reliability of NMR?

Example : $N = 5$

$$R_{\text{NMR}} = \left[C_5^3 p^3 (1-p)^2 + C_5^4 p^4 (1-p) + C_5^5 p^5 \right] \cdot w$$
$$= \left(\sum_{i=3}^5 C_5^i p^i (1-p)^{5-i} \right) \cdot w$$

In general.

$$R = \left(\sum_{i=n+1}^N C_N^i p^i (1-p)^{N-i} \right) \cdot w$$

$$C_N^i = \binom{N}{i} = \frac{N!}{i!(N-i)!}$$

Voting Techniques in NMR

- Hardware voting & software voting
- Hardware voting uses a hardware voter
 - Logic gates, using digital logic design technique
- Exercise: design a 1-bit TMR voter that produces an output of 1 when 2 out of 3 inputs are 1
 - Truth table?
 - Karnaugh map?
 - Logic function for the voter?
 - Implementation: circuit?

Dr. Xing

Lecture #4

15

①

Input			output
A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



$$F = \bar{A} \cdot B \cdot C + A \bar{B} C + A B \bar{C} + A B C \quad (\text{Top circuit in slide \#16})$$

② Simplification using - K-map

	0	1	1	0
BC	00	01	11	10
A	0	0	1	0
1	0	1	1	1

$$F = AB + AC + BC \quad (\text{Bottom circuit in slide \#16})$$

Implementation Circuits

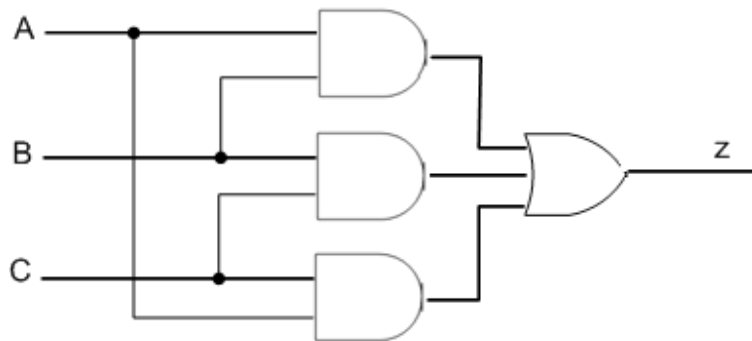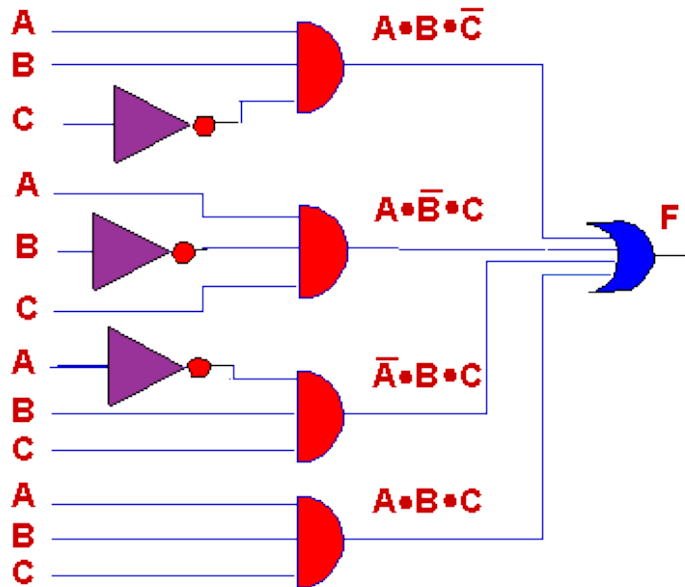

An 8-bit or 16-bit majority voter can be constructed using 8 or 16 of the above circuits