

ECE454/544: Fault-Tolerant Computing & Reliability Engineering
(Fall 2022)

Homework #3 Solution

(50 points)

1. **(30 points) Non-separable Cyclic Code:**

1) Design a combinatorial circuit that is capable of encoding four-bit information words into *non-separable* cyclic code words using the generator polynomial $G(X)=1+X+X^2+X^5$. **(20 points)**

2) Show the resulting code word for the data word $(d_3 d_2 d_1 d_0) = (1011)$. **(10 points)**

Solution:

$$\left. \begin{array}{l} \text{Information words: 4 bits} \Rightarrow k=4 \\ G(x) = 1+x+x^2+x^5 \Rightarrow n-k=5 \end{array} \right\} \Rightarrow n=9$$

$$\text{Data polynomial: } D(x) = d_0 + d_1x + d_2x^2 + d_3x^3$$

$$\text{Generator polynomial: } G(x) = 1 + x + x^2 + x^5$$

$$\text{Code polynomial: } V(x) = D(x) \cdot G(x) = v_0 + v_1x + v_2x^2 + \dots + v_8x^8$$

$$V(x) = D(x) \cdot G(x) = (d_0 + d_1x + d_2x^2 + d_3x^3) (1 + x + x^2 + x^5)$$

$$= d_0 + d_0x + d_0x^2 + d_0x^5 + d_1x + d_1x^2 + d_1x^3 + d_1x^6 +$$

$$d_2x^2 + d_2x^3 + d_2x^4 + d_2x^7 + d_3x^3 + d_3x^4 + d_3x^5 + d_3x^8$$

$$= d_0 + (d_0 + d_1)x + (d_0 + d_1 + d_2)x^2 + (d_1 + d_2 + d_3)x^3 + (d_2 + d_3)x^4$$


$$+ (d_0 + d_3)x^5 + d_1x^6 + d_2x^7 + d_3x^8$$

So, the code word is given by:

$$v = (v_0, v_1, v_2, v_3, v_4, v_5, v_6, v_7, v_8)$$

$$= (d_0, (d_0 + d_1), (d_0 + d_1 + d_2), (d_1 + d_2 + d_3), (d_2 + d_3), (d_0 + d_3), d_1, d_2, d_3)$$

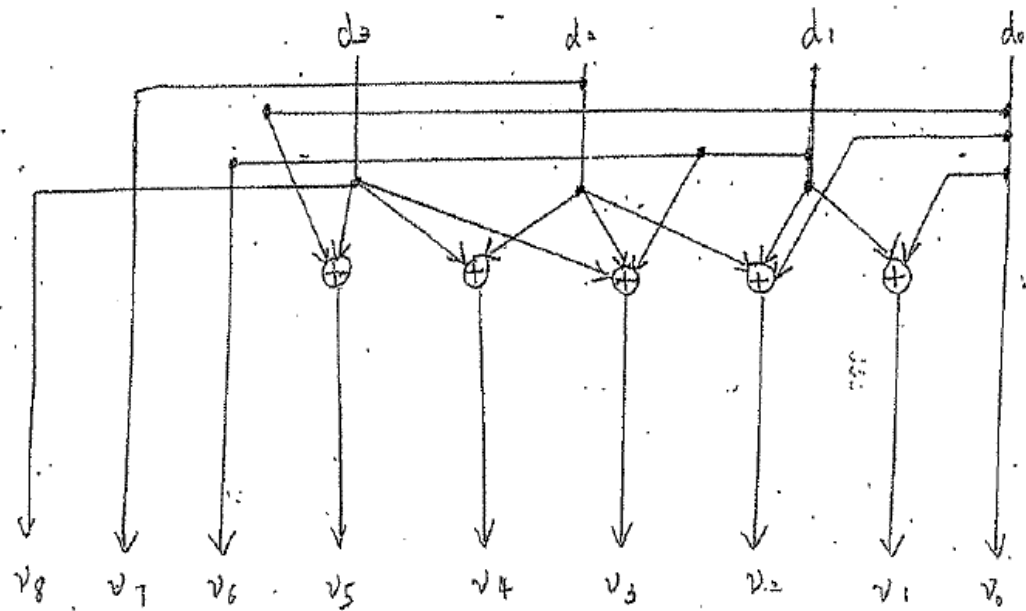Thus, this non-separable cyclic code can be implemented using the following combinatorial circuit composed of EXCLUSIVE-OR gates only:



\oplus : EXCLUSIVE-OR gate implementing modulo-2 addition

For data word 1011 we have

$$D(x) = 1 + x + x^3$$

$$V(x) = D(x) \cdot E(x) = (1 + x + x^3)(1 + x + x^2 + x^5)$$

$$= 1 + x^4 + x^6 + x^8$$

So, the code word for 1011 is

$$v = (v_8, v_7, \dots, v_1, v_0)$$

$$= (101010001)$$

2. (20 points) **Separable Cyclic Code:**

Show the *separable* cyclic code word for the data word $(d_3 d_2 d_1 d_0) = (1011)$ using the generator polynomial $G(X) = 1 + X + X^2 + X^5$.

Solution:

For data word 1011, we have

$$D(X) = 1 + X + X^3$$

To construct separable cyclic code, we compute:

$$\textcircled{1} X^{n-k} \cdot D(X) = X^5 (1 + X + X^3) = X^5 + X^6 + X^8$$

\textcircled{2} Find the remainder $R(X)$ of the division $X^{n-k} D(X) / G(X)$

$$\begin{array}{r} X^3 + X \\ X^5 + X^2 + X + 1 \overline{) X^8 + X^6 + X^5} \\ \underline{X^8 + X^5 + X^4 + X^3} \\ X^6 + X^4 + X^3 \\ \underline{X^6 + X^3 + X^2 + X} \\ X^4 + X^2 + X \rightarrow R(X) \end{array}$$

$$\text{So, } R(X) = X^4 + X^2 + X$$

$$\begin{aligned} \textcircled{3} V(X) &= X^{n-k} D(X) + R(X) = X^5 + X^6 + X^8 + X^4 + X^2 + X \\ &= X^8 + X^6 + X^5 + X^4 + X^2 + X \end{aligned}$$

So, the separate cyclic code word for 1011 is:

$$\begin{aligned} v &= (v_8, v_7, \dots, v_1, v_0) \\ &= (101110110) \end{aligned}$$